

Lab 2: Design of Data Paths and Control Units Using VHDL

University of Guelph
ENGG*3050 Winter 2016
Professor Shawki Areibi

Graham Thoms 0795111
Vithursan Thangarasa 0821795

1 Introduction

This lab required the use of VHDL to be used as tool for design entry and design the following circuits:

- 4-Bit Algorithmic Logic Unit (ALU)
- 4 x 4 Binary Multiplier using Repeated Addition

The circuits were then tested and debugged by mapping on to the NEXYS3 Spartan-6 FPGA board, and performing simulations using Xilinx ISE Simulator.

2 Summary of Circuit Designs

This section outlines the preliminary work, implementation approaches, and simulation results of the respective circuits.

2.1 4-Bit Algorithmic Logic Unit

2.1.1 Truth Table for Specified ALU

The table presented in **Table 1** is the truth table for the required Algorithmic Logic Unit (ALU). The block diagram for the 1-bit ALU is depicted in **Figure 1**.

Table 1 Shows the truth table of the specified ALU.

Cin	S1	S0	F	X	Y
0	0	0	A + B	A	B
0	0	1	(not A) + B	not A	B
0	1	0	A - 1	A	1
0	1	1	not A	Not A	0
1	0	0	A - B	A	not B
1	0	1	B - A	Not A	B
1	1	0	A + 1	A	0
1	1	1	(not A) + 1	Not A	0

2.1.2 1-Bit Algorithmic Logic Unit

Inputs A and B were sent through a 8 to 1 bit multiplexers and into a 1 bit full adder in order to have various arithmetic operations shown in **Table 1**. These logic operations were synthesized into **Figure 1** to give the specified 1-bit Arithmetic Logic Unit. VHDL Implementation can be found in **Appendix A**.

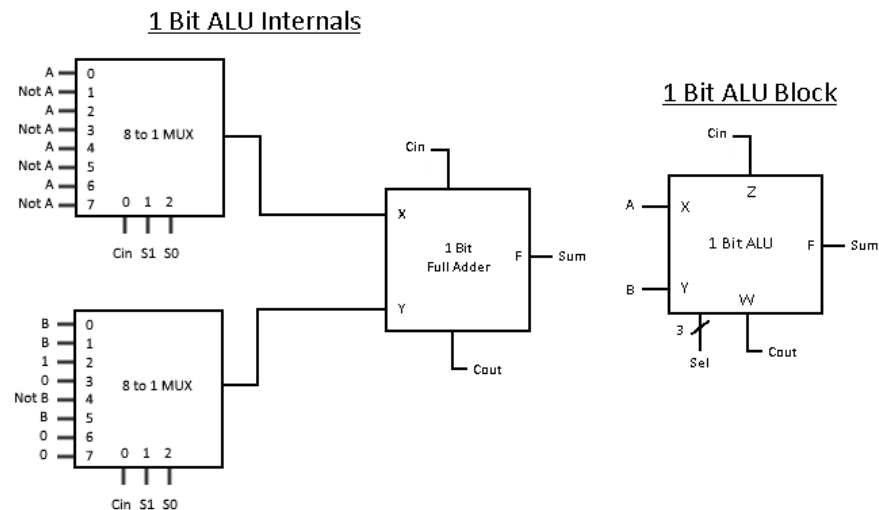


Figure 1 Shows the implementation of the 1-bit ALU

In **Figure 2** sample inputs $a = 1$ and $b = 0$ were used to run through each arithmetic operation using the select lines $sel[2:0] = \{S1, S0, Cin\}$. For example $sel = "110"$ is the operation 1s complement of A, thus the result is 0, which is shown in the above figure. VHDL Implementation of the test bench can be found in **Appendix B**.

 


Figure 2 Shows the logic waveform of the 1 bit ALU.

2.1.3 Implementation Approach 4-Bit ALU

The 1-Bit ALU was repeated 4 times to create the 4-Bit ALU as shown in **Figure 3**. It comprises of 4 1-bit ALUs that are cascaded into the next bit and produce the logic operations shown in **Table 1** for two 4 bit numbers. VHDL implementation can be found in **Appendix C**. The 4-bit ALU outputted a binary coded decimal that was imported to a 7-Segment display, as well as the LEDs.

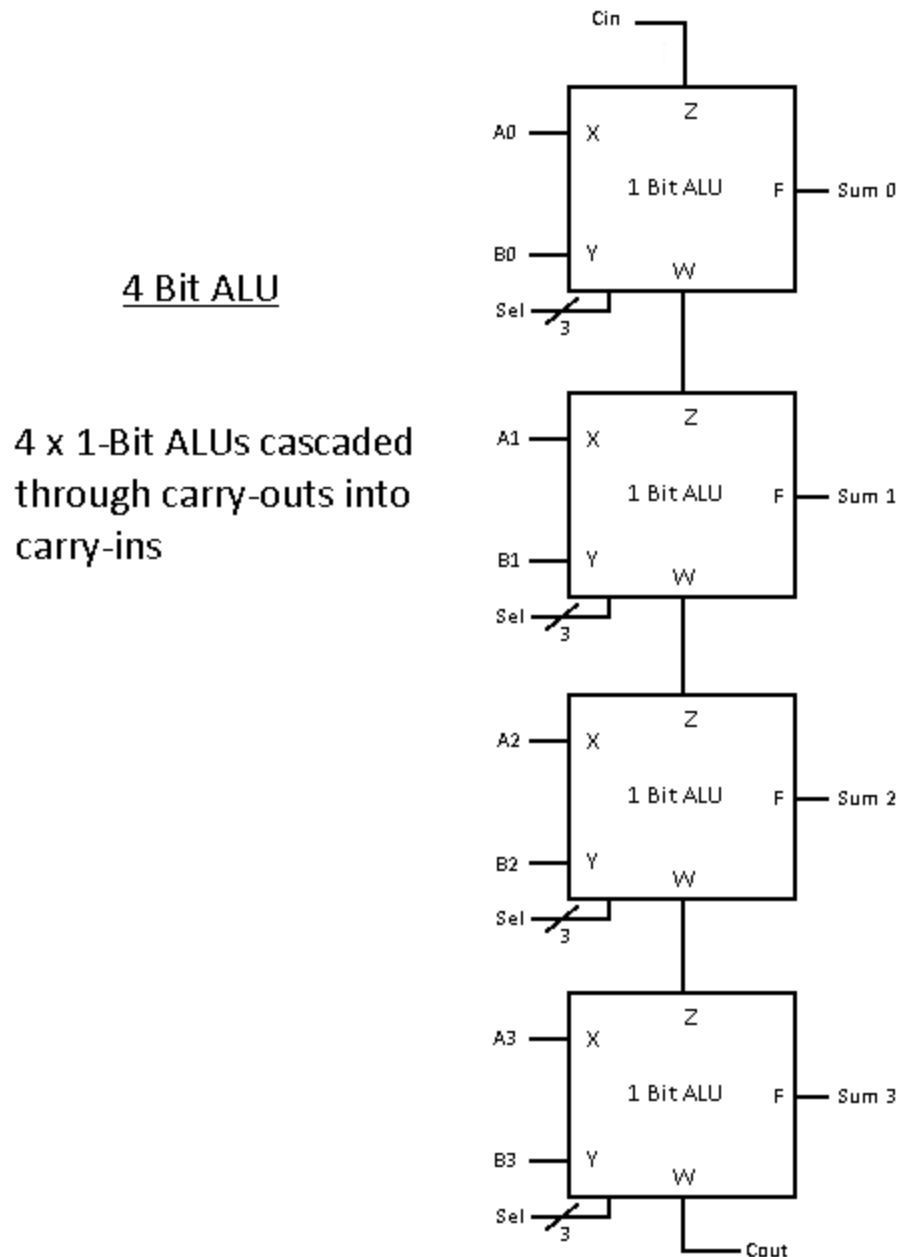


Figure 3 Block diagram of the 4-Bit ALU.

2.1.4 Testbench of 4-Bit ALU

In **Figure 4**, sample inputs $a = 6$ and $b = 2$ were used to run through each arithmetic operation using the select lines $sel[2:0] = \{S1, S0, Cin\}$. For example $sel = "001"$ is the operation $a - b$, thus in this case $6 - 2 = 4$ (100), which is shown in the above figure. VHDL Implementation can be found in **Appendix D**.

 


Figure 4 Shows the logic waveform of the specified 4-bit ALU.

2.3 4-Bit Multiplication Unit

2.3.1 Implementation Approach 4 x 4 Multiplier

The ASM chart for the 4 x 4 Multiplier is presented in **Figure 6**. The datapath circuit for the multiplier is presented in **Figure 7**. The ASM chart for the multiplier control unit is presented in **Figure 8**. The multiplicand is 4-bit wide (BR) and the multiplier (AR) is 4-bit wide, thus the product will need an 8-bit register (double width register). The multiplier is placed in the least significant half of the product register (PR), and the most significant half of the PR is cleared. Since there are 4 bits in a single width register, the following steps were performed 4 times:

1. If the least significant bit (LSB) of the product register (PR) contains a 1, the multiplicand is added to the most significant half
2. The whole register is shifted one bit to the right, thus discard the least significant bit. This also shifts the carry bit into the most significant bit.

The VHDL code for the 4 x 4 Multiplier using the Adder and Shifter is presented in **Appendix E**.

 


Figure 6 An ASM chart for the multiplier

 


Figure 7 Datapath circuit for the multiplier.

 


Figure 8 An ASM chart for the multiplier control unit.

2.3.2 Testbench for 4-Bit Multiplication Unit

The testbench simulation result for the 4-bit multiplication unit presented in a wave diagram shown in **Figure 9**. The start button is set to HIGH to activate the control unit. The input A vector is “1111” and the input B vector is “1111”, which resulted in an output of “11100001”. This output is correct as shown in **Figure 10**. For the second test, the input vector A is “1001” and the input vector B is “1111”, which resulted in an output of “01010001”. The output is also correct as shown in **Figure 11**. The test bench code is provided in **Appendix F**.



Figure 9 Simulation waveform for the 4 x 4 Multiplier.

$$\begin{array}{r}
 1111 \\
 \times 1111 \\
 \hline
 1111 \\
 11110 \\
 111100 \\
 1111000 \\
 \hline
 11100001
 \end{array}$$

$$\begin{array}{r}
 15 \\
 \times 15 \\
 \hline
 225
 \end{array}$$

$$\begin{aligned}
 &= 2^7 + 2^6 + 2^5 + 2^0 \\
 &= 128 + 64 + 32 + 1 \\
 &= 225
 \end{aligned}$$

Figure 10 Expected Output where input A = “1111” and B = “1111”. The output is “11100001”.

$$\begin{array}{r}
 1001 \\
 \times 1001 \\
 \hline
 1001 \\
 10010 \\
 100100 \\
 1001000 \\
 \hline
 01010001
 \end{array}$$

$$\begin{array}{r}
 9 \\
 \times 9 \\
 \hline
 81
 \end{array}$$

$$\begin{aligned}
 &= 2^3 + 2^4 + 2^0 \\
 &= 64 + 16 + 1 \\
 &= 81
 \end{aligned}$$

Figure 11 Expected output where input A = “1001” and B = “1001”. The output is “01010001”.

3 Conclusion and Future Considerations

In the final analysis, this lab helped develop a stronger understanding of the internal components in an ALU and Multiplier, create ASM charts, implementing state machines in VHDL, and using Xilinx ISE Design to map and simulate the circuits. This lab served as a beneficial tool with getting familiar with fundamental VHDL concepts. In the future, it may help to review VHDL programming concepts and styles, especially implementing registers, state processes, components, and etc. to give some background before beginning the lab.

Appendix A

ALU_1bit.vhd

Mon Feb 01 23:59:20 2016

```
1  -----
2  -- Company:
3  -- Engineer: Graham Thoms
4  --
5  -- Create Date:    14:36:12 01/31/2016
6  -- Design Name:
7  -- Module Name:    alu_VHDL - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32
33
34 -----
35 --                                1 bit ALU
36 -----
37
38
39 entity alu_VHDL_1bit is
40     Port ( A : in  STD_LOGIC;
41           B : in  STD_LOGIC;
42           S : out STD_LOGIC;
43           Cin : in  STD_LOGIC;
44           Cout : out STD_LOGIC;
45           SEL : in  STD_LOGIC_VECTOR (2 downto 0));
46 end alu_VHDL_1bit;
47
48 architecture Behavioral of alu_VHDL_1bit is
49
50     component FullAdder is
51         Port ( x : in  STD_LOGIC;
52               y : in  STD_LOGIC;
53               g : out STD_LOGIC;
54               ci : in  STD_LOGIC;
55               co : out STD_LOGIC);
56     end component;
57
```

```

58     component Mux8to1 is
59         Port ( b0 : in  STD_LOGIC;
60               b1 : in  STD_LOGIC;
61               b2 : in  STD_LOGIC;
62               b3 : in  STD_LOGIC;
63               b4 : in  STD_LOGIC;
64               b5 : in  STD_LOGIC;
65               b6 : in  STD_LOGIC;
66               b7 : in  STD_LOGIC;
67               sel: in  STD_LOGIC_VECTOR(2 downto 0);
68               dout : out STD_LOGIC);
69     end component;
70
71     signal S_s, Co_s, dout_s_a, dout_s_b : STD_LOGIC;
72
73     begin
74
75         -- connecting MUXs for inputs a and b to fulladder
76
77         A0: Mux8to1 port map (A, A,not A,not A,A, A, not A, not A, Sel, dout_s_a);
78         B0: Mux8to1 port map (B, not B,B,B,'1', '0', '0', '0', Sel, dout_s_b);
79         F0: FullAdder port map (dout_s_a, dout_s_b, S_s, Cin, Co_s);
80
81         -- outputs of 1 bit ALU
82
83         S <= S_s;
84         Cout <= Co_s;
85
86     end Behavioral;
87
88     -----
89     --                                     END 1 bit ALU
90     -----
91
92     -----
93     --                                     FULL ADDER
94     -----
95
96     library IEEE;
97     use IEEE.STD_LOGIC_1164.ALL;
98
99     entity FullAdder is
100         Port ( x : in  STD_LOGIC;           -- input x
101               y : in  STD_LOGIC;           -- input y
102               g : out STD_LOGIC;           -- output g = x + y + ci
103               ci : in  STD_LOGIC;          -- input ci (carry in)
104               co : out STD_LOGIC);          -- output co (carry out)
105     end FullAdder;
106
107     architecture dataflow of FullAdder is
108     begin
109
110         -- fulladder logic
111
112         g <= ((x xor y) xor ci);           -- sum
113         co <= ((x and y) or ((x xor y) and ci)); -- carry out
114

```

```
115 end dataflow;
116
117 -----
118 --                                END FULL ADDER
119 -----
120
121 -----
122 --                                8 to 1 MUX
123 -----
124
125 library IEEE;
126 use IEEE.STD_LOGIC_1164.ALL;
127
128 entity Mux8to1 is
129     Port ( b0 : in  STD_LOGIC;           -- MUX inputs
130           b1 : in  STD_LOGIC;
131           b2 : in  STD_LOGIC;
132           b3 : in  STD_LOGIC;
133           b4 : in  STD_LOGIC;
134           b5 : in  STD_LOGIC;
135           b6 : in  STD_LOGIC;
136           b7 : in  STD_LOGIC;
137           sel : in STD_LOGIC_VECTOR(2 downto 0); -- select lines
138           dout : out STD_LOGIC);               -- output
139 end Mux8to1;
140
141 architecture Behavioral of Mux8to1 is
142     begin
143
144         -- behaviour of 8 to 1 MUX
145
146         dout <=      b0 when (sel="000")
147                     else
148                     b1 when (sel="001")
149                     else
150                     b2 when (sel="010")
151                     else
152                     b3 when (sel="011")
153                     else
154                     b4 when (sel="100")
155                     else
156                     b5 when (sel="101")
157                     else
158                     b6 when (sel="110")
159                     else
160                     b7;
161     end Behavioral;
162
163 -----
164 --                                END 8 to 1 MUX
165 -----
166
167
168
169
170
```

Appendix B

ALU_1bit_TB.vhd

Mon Feb 01 23:58:29 2016

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    23:45:36 02/01/2016
6  -- Design Name:
7  -- Module Name:    T:/ENGG3050/ALU_1bit/ALU_1bit_TB.vhd
8  -- Project Name:   ALU_1bit
9  -- Target Device:
10 -- Tool versions:
11 -- Description:
12 --
13 -- VHDL Test Bench Created by ISE for module: alu_VHDL_1bit
14 --
15 -- Dependencies:
16 --
17 -- Revision:
18 -- Revision 0.01 - File Created
19 -- Additional Comments:
20 --
21 -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
23 -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
25 -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
27 -----
28 LIBRARY ieee;
29 USE ieee.std_logic_1164.ALL;
30
31 -- Uncomment the following library declaration if using
32 -- arithmetic functions with Signed or Unsigned values
33 --USE ieee.numeric_std.ALL;
34
35 ENTITY ALU_1bit_TB IS
36 END ALU_1bit_TB;
37
38 ARCHITECTURE behavior OF ALU_1bit_TB IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT alu_VHDL_1bit
43     PORT(
44         A : IN  std_logic;
45         B : IN  std_logic;
46         S : OUT std_logic;
47         Cin : IN std_logic;
48         Cout : OUT std_logic;
49         SEL : IN std_logic_vector(2 downto 0)
50     );
51     END COMPONENT;
52
53
54 --Inputs
55 signal A : std_logic := '0';
56 signal B : std_logic := '0';
57 signal Cin : std_logic := '0';
```

```

58     signal SEL : std_logic_vector(2 downto 0) := (others => '0');
59
60     --Outputs
61     signal S : std_logic;
62     signal Cout : std_logic;
63     -- No clocks detected in port list. Replace <clock> below with
64     -- appropriate port name
65
66     constant period : time := 10 ns;
67
68 BEGIN
69
70     -- Instantiate the Unit Under Test (UUT)
71     uut: alu_VHDL_lbit PORT MAP (
72         A => A,
73         B => B,
74         S => S,
75         Cin => Cin,
76         Cout => Cout,
77         SEL => SEL
78     );
79
80
81
82     -- Stimulus process
83     stim_proc: process
84     begin
85         wait for period;
86
87         A <= '1'; -- a = 1 (0110)
88         B <= '0'; -- b = 2 (0010)
89         Cin <= '0';
90
91         -- SEL(0) = Cin
92
93         -- SEL(0)|SEL(2)|SEL(1) | F
94         -----
95         -- 0      0      0   | a + b
96         -----
97         -- 0      0      1   | (not a) + b
98         -----
99         -- 0      1      0   | a - 1
100        -----
101        -- 0      1      1   | not a
102        -----
103        -- 1      0      0   | a - b
104        -----
105        -- 1      0      1   | b - a
106        -----
107        -- 1      1      0   | a + 1
108        -----
109        -- 1      1      1   | (not a) + b
110        -----
111
112        -- operations 0 - 3
113
114        SEL(0) <= '0'; --OPERATION: a + b

```

```
115     SEL(2) <= '0';
116     SEL(1) <= '0'; -- RESULT = 1
117
118     wait for period;
119
120     SEL(0) <= '0'; --OPERATION: (not a) + b
121     SEL(2) <= '0';
122     SEL(1) <= '1'; -- RESULT = 0
123
124     wait for period;
125
126     SEL(0) <= '0'; --OPERATION: a - 1
127     SEL(2) <= '1';
128     SEL(1) <= '0'; -- RESULT = 0
129
130     wait for period;
131
132     SEL(0) <= '0'; --OPERATION: not a , 1s complement
133     SEL(2) <= '1';
134     SEL(1) <= '1'; -- RESULT = 0
135
136     wait for period;
137
138     -- operations 4 - 7
139
140     SEL(0) <= '1'; --OPERATION: a - b
141     SEL(2) <= '0';
142     SEL(1) <= '0'; -- RESULT = 1
143     Cin <= '1';
144
145     wait for period;
146
147     SEL(0) <= '1'; --OPERATION: b - a
148     SEL(2) <= '0';
149     SEL(1) <= '1'; -- RESULT = 0
150     Cin <= '1';
151
152     wait for period;
153
154     SEL(0) <= '1'; --OPERATION: a + 1
155     SEL(2) <= '1';
156     SEL(1) <= '0'; -- RESULT = 0
157     Cin <= '1';
158
159     wait for period;
160
161     SEL(0) <= '1'; --OPERATION: not a + 1 , 2s complement
162     SEL(2) <= '1';
163     SEL(1) <= '1'; -- RESULT = 1
164     Cin <= '1';
165
166     wait for period;
167
168
169     wait for period;
170
171     wait;
```

```
172     end process;
173
174     END;
175
```

Appendix C

alu_VHDL.vhd

Mon Feb 01 23:01:42 2016

```
1  -----
2  -- Company:
3  -- Engineer: Graham Thoms
4  --
5  -- Create Date:    14:36:12 01/31/2016
6  -- Design Name:
7  -- Module Name:    alu_VHDL - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 -----
33 --                                4 bit ALU
34 -----
35
36 entity alu_VHDL_4bit is                                -- entity for 4 bit ALU
37     Port ( a : in STD_LOGIC_VECTOR(3 downto 0);        -- input a
38           b : in STD_LOGIC_VECTOR(3 downto 0);        -- input b
39           SEL:in STD_LOGIC_VECTOR(2 downto 0);        -- select lines
40           ci : in STD_LOGIC;                          -- carry in
41           co : out STD_LOGIC;                         -- carry out
42           S : out STD_LOGIC_VECTOR(3 downto 0);        -- binary output
43           SS : out STD_LOGIC_VECTOR(6 downto 0);      -- 7 segment display output
44           Aout: out STD_LOGIC_VECTOR(3 downto 0);    -- A output for leds
45           Bout: out STD_LOGIC_VECTOR(3 downto 0);    -- B output for leds
46           POS : out STD_LOGIC_VECTOR(3 downto 0));    -- display digit select
47 end alu_VHDL_4bit;
48
49 architecture Behavioral of alu_VHDL_4bit is
50
51     component alu_VHDL_1bit is
52     Port ( A : in  STD_LOGIC;
53           B : in  STD_LOGIC;
54           S : out  STD_LOGIC;
55           Cin : in  STD_LOGIC;
56           Cout : out STD_LOGIC;
57           sel : in STD_LOGIC_VECTOR (2 downto 0));
```



```
58     end component;
59
60     component SevenSeg is
61         Port (   BCD : in STD_LOGIC_VECTOR(3 downto 0); -- Binary coded decimal input
62                 SevenSegDisplay : out STD_LOGIC_VECTOR(6 downto 0));
63     end component;
64
65
66     signal S_one, S_two, S_three, S_four: std_logic;
67     signal C_one, C_two, C_three, C_four: std_logic;
68     signal gout : STD_LOGIC_VECTOR(3 downto 0);
69
70     begin
71
72         -- 4 x 1 bit ALUs cascaded through the carry-outs to the carry-ins
73
74         G0: alu_VHDL_1bit port map (a(0), b(0), S_one, SEL(0), C_one, SEL);
75         G1: alu_VHDL_1bit port map (a(1), b(1), S_two, C_one, C_two, SEL);
76         G2: alu_VHDL_1bit port map (a(2), b(2), S_three, C_two, C_three, SEL);
77         G3: alu_VHDL_1bit port map (a(3), b(3), S_four, C_three, C_four, SEL);
78
79         -- Operands to LEDs
80
81         Aout(0) <= a(0);
82         Aout(1) <= a(1);
83         Aout(2) <= a(2);
84         Aout(3) <= a(3);
85         Bout(0) <= b(0);
86         Bout(1) <= b(1);
87         Bout(2) <= b(2);
88         Bout(3) <= b(3);
89
90         -- 4 bit sum
91
92         gout(0) <= S_one;
93         gout(1) <= S_two;
94         gout(2) <= S_three;
95         gout(3) <= S_four;
96         co <= C_four;
97
98         S(0) <= S_one;
99         S(1) <= S_two;
100        S(2) <= S_three;
101        S(3) <= S_four;
102
103        -- seven segment display outputting 4 bit sum
104
105        POS <= "1110";
106
107        U1: SevenSeg port map (gout,SS);
108
109    end Behavioral;
110
111    -----
112    --                                     END 4 bit ALU
113    -----
114
```

```

115 -----
116 --                                1 bit ALU
117 -----
118 library IEEE;
119 use IEEE.STD_LOGIC_1164.ALL;
120
121
122 entity alu_VHDL_1bit is
123     Port ( A : in  STD_LOGIC;
124           B : in  STD_LOGIC;
125           S : out  STD_LOGIC;
126           Cin : in  STD_LOGIC;
127           Cout : out  STD_LOGIC;
128           SEL : in  STD_LOGIC_VECTOR (2 downto 0));
129 end alu_VHDL_1bit;
130
131 architecture Behavioral of alu_VHDL_1bit is
132
133     component FullAdder is
134         Port ( x : in  STD_LOGIC;
135               y : in  STD_LOGIC;
136               g : out  STD_LOGIC;
137               ci : in  STD_LOGIC;
138               co : out  STD_LOGIC);
139     end component;
140
141     component Mux8to1 is
142         Port ( b0 : in  STD_LOGIC;
143               b1 : in  STD_LOGIC;
144               b2 : in  STD_LOGIC;
145               b3 : in  STD_LOGIC;
146               b4 : in  STD_LOGIC;
147               b5 : in  STD_LOGIC;
148               b6 : in  STD_LOGIC;
149               b7 : in  STD_LOGIC;
150               sel: in  STD_LOGIC_VECTOR(2 downto 0);
151               dout : out  STD_LOGIC);
152     end component;
153
154     signal S_s, Co_s, dout_s_a, dout_s_b : STD_LOGIC;
155
156     begin
157
158         -- connecting MUXs for inputs a and b to fulladder
159
160         A0: Mux8to1 port map (A, A,not A,not A,A, A, not A, not A, Sel, dout_s_a);
161         B0: Mux8to1 port map (B, not B,B,B,'1', '0', '0', '0', Sel, dout_s_b);
162         F0: FullAdder port map (dout_s_a, dout_s_b, S_s, Cin, Co_s);
163
164         -- outputs of 1 bit ALU
165
166         S <= S_s;
167         Cout <= Co_s;
168
169     end Behavioral;
170
171 -----

```

```

172  --                                END 1 bit ALU
173  -----
174
175  -----
176  --                                FULL ADDER
177  -----
178
179  library IEEE;
180  use IEEE.STD_LOGIC_1164.ALL;
181
182  entity FullAdder is
183      Port ( x : in  STD_LOGIC;           -- input x
184            y : in  STD_LOGIC;           -- input y
185            g : out STD_LOGIC;           -- output g = x + y + ci
186            ci : in  STD_LOGIC;           -- input ci (carry in)
187            co : out STD_LOGIC);          -- output co (carry out)
188  end FullAdder;
189
190  architecture dataflow of FullAdder is
191      begin
192
193          -- fulladder logic
194
195          g <= ((x xor y) xor ci);         -- sum
196          co <= ((x and y) or ((x xor y) and ci)); -- carry out
197
198      end dataflow;
199
200  -----
201  --                                END FULL ADDER
202  -----
203
204  -----
205  --                                8 to 1 MUX
206  -----
207
208  library IEEE;
209  use IEEE.STD_LOGIC_1164.ALL;
210
211  entity Mux8to1 is
212      Port ( b0 : in  STD_LOGIC;           -- MUX inputs
213            b1 : in  STD_LOGIC;
214            b2 : in  STD_LOGIC;
215            b3 : in  STD_LOGIC;
216            b4 : in  STD_LOGIC;
217            b5 : in  STD_LOGIC;
218            b6 : in  STD_LOGIC;
219            b7 : in  STD_LOGIC;
220            sel : in STD_LOGIC_VECTOR(2 downto 0); -- select lines
221            dout : out STD_LOGIC);          -- output
222  end Mux8to1;
223
224  architecture Behavioral of Mux8to1 is
225      begin
226
227          -- behaviour of 8 to 1 MUX
228

```

```

229     dout <=      b0 when (sel="000")
230                else
231                b1 when (sel="001")
232                else
233                b2 when (sel="010")
234                else
235                b3 when (sel="011")
236                else
237                b4 when (sel="100")
238                else
239                b5 when (sel="101")
240                else
241                b6 when (sel="110")
242                else
243                b7;
244 end Behavioral;
245
246 -----
247 --                                END 8 to 1 MUX
248 -----
249
250 -----
251 --                                7 SEG DISPLAY
252 -----
253
254 library IEEE;
255 use IEEE.STD_LOGIC_1164.ALL;
256
257 entity SevenSeg is
258     Port (
259         BCD : in STD_LOGIC_VECTOR(3 downto 0);           -- Binary coded decimal input
260         SevenSegDisplay : out STD_LOGIC_VECTOR(6 downto 0) -- 7 seg display output
261     );
262 end SevenSeg;
263
264 architecture Behavioral of SevenSeg is
265
266     begin
267
268     process(BCD)
269     BEGIN
270
271         case BCD is -- input for the LCD Display, allows user to visually see the number
272         on a screen
273             when "0000"=> SevenSegDisplay <="0000001"; -- '0'
274             when "0001"=> SevenSegDisplay <="1001111"; -- '1'
275             when "0010"=> SevenSegDisplay <="0010010"; -- '2'
276             when "0011"=> SevenSegDisplay <="0000110"; -- '3'
277             when "0100"=> SevenSegDisplay <="1001100"; -- '4'
278             when "0101"=> SevenSegDisplay <="0100100"; -- '5'
279             when "0110"=> SevenSegDisplay <="0100000"; -- '6'
280             when "0111"=> SevenSegDisplay <="0001111"; -- '7'
281             when "1000"=> SevenSegDisplay <="0000000"; -- '8'
282             when "1001"=> SevenSegDisplay <="0000100"; -- '9'
283             when "1010"=> SevenSegDisplay <="0001000"; -- 'A'
284             when "1011"=> SevenSegDisplay <="1100000"; -- 'b'
285             when "1100"=> SevenSegDisplay <="0110001"; -- 'C'

```

```
285     when "1101" => SevenSegDisplay <="1000010"; -- 'd'
286     when "1110" => SevenSegDisplay <="0110000"; -- 'E'
287     when "1111" => SevenSegDisplay <="0111000"; -- 'F'
288     when others => SevenSegDisplay <="1111111";-- ERROR
289   end case;
290
291 end process;
292
293 end Behavioral;
294
295 -----
296 --                               END 7 SEG DISPLAY
297 -----
298
299
300
```

Appendix D

ALU_VHDL_TB.vhd

Mon Feb 01 23:03:08 2016

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    22:05:43 02/01/2016
6  -- Design Name:
7  -- Module Name:    H:/ENGG3050/ALU_VHDL/ALU_VHDL_TB.vhd
8  -- Project Name:   ALU_VHDL
9  -- Target Device:
10 -- Tool versions:
11 -- Description:
12 --
13 -- VHDL Test Bench Created by ISE for module: alu_VHDL_4bit
14 --
15 -- Dependencies:
16 --
17 -- Revision:
18 -- Revision 0.01 - File Created
19 -- Additional Comments:
20 --
21 -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
23 -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
25 -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
27 -----
28 LIBRARY ieee;
29 USE ieee.std_logic_1164.ALL;
30
31 -- Uncomment the following library declaration if using
32 -- arithmetic functions with Signed or Unsigned values
33 --USE ieee.numeric_std.ALL;
34
35 ENTITY ALU_VHDL_TB IS
36 END ALU_VHDL_TB;
37
38 ARCHITECTURE behavior OF ALU_VHDL_TB IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT alu_VHDL_4bit
43     PORT(
44         a : IN  std_logic_vector(3 downto 0);
45         b : IN  std_logic_vector(3 downto 0);
46         SEL : IN  std_logic_vector(2 downto 0);
47         ci : IN  std_logic;
48         co : OUT std_logic;
49         S : OUT std_logic_vector(3 downto 0);
50         SS : OUT std_logic_vector(6 downto 0);
51         Aout : OUT std_logic_vector(3 downto 0);
52         Bout : OUT std_logic_vector(3 downto 0);
53         POS : OUT std_logic_vector(3 downto 0)
54     );
55     END COMPONENT;
56
57
```

```

58  --Inputs
59  signal a : std_logic_vector(3 downto 0) := (others => '0');
60  signal b : std_logic_vector(3 downto 0) := (others => '0');
61  signal SEL : std_logic_vector(2 downto 0) := (others => '0');
62  signal ci : std_logic := '0';
63
64  --Outputs
65  signal co : std_logic;
66  signal S : std_logic_vector(3 downto 0);
67  signal SS : std_logic_vector(6 downto 0);
68  signal Aout : std_logic_vector(3 downto 0);
69  signal Bout : std_logic_vector(3 downto 0);
70  signal POS : std_logic_vector(3 downto 0);
71  -- No clocks detected in port list. Replace <clock> below with
72  -- appropriate port name
73
74  constant period : time := 10 ns;
75
76  BEGIN
77
78  -- Instantiate the Unit Under Test (UUT)
79  uut: alu_VHDL_4bit PORT MAP (
80      a => a,
81      b => b,
82      SEL => SEL,
83      ci => ci,
84      co => co,
85      S => S,
86      SS => SS,
87      Aout => Aout,
88      Bout => Bout,
89      POS => POS
90  );
91
92
93  -- Stimulus process
94  stim_proc: process
95  begin
96      wait for period;
97
98      a(3) <= '0'; -- a = 6 (0110)
99      a(2) <= '1';
100     a(1) <= '1';
101     a(0) <= '0';
102
103     b(3) <= '0'; -- b = 2 (0010)
104     b(2) <= '0';
105     b(1) <= '1';
106     b(0) <= '0';
107
108     -- SEL(0) = Cin
109
110     -- SEL(0)|SEL(2)|SEL(1) | F
111     -----
112     --  0      0      0    | a + b
113     -----
114     --  0      0      1    | (not a) + b

```

```
115      -----
116      --  0      1      0      | a - 1
117      -----
118      --  0      1      1      | not a
119      -----
120      --  1      0      0      | a - b
121      -----
122      --  1      0      1      | b - a
123      -----
124      --  1      1      0      | a + 1
125      -----
126      --  1      1      1      | (not a) + b
127      -----
128
129      -- operations 0 - 3
130
131      SEL(0) <= '0'; --OPERATION: a + b
132      SEL(2) <= '0';
133      SEL(1) <= '0'; -- RESULT = 8
134
135      wait for period;
136
137      SEL(0) <= '0'; --OPERATION: (not a) + b
138      SEL(2) <= '0';
139      SEL(1) <= '1'; -- RESULT = B
140
141      wait for period;
142
143      SEL(0) <= '0'; --OPERATION: a - 1
144      SEL(2) <= '1';
145      SEL(1) <= '0'; -- RESULT = 5
146
147      wait for period;
148
149      SEL(0) <= '0'; --OPERATION: not a , 1s complement
150      SEL(2) <= '1';
151      SEL(1) <= '1'; -- RESULT = 9
152
153      wait for period;
154
155
156
157      -- operations 4 - 7
158
159      SEL(0) <= '1'; --OPERATION: a - b
160      SEL(2) <= '0';
161      SEL(1) <= '0'; -- RESULT = 4
162
163      wait for period;
164
165      SEL(0) <= '1'; --OPERATION: b - a
166      SEL(2) <= '0';
167      SEL(1) <= '1'; -- RESULT = C
168
169      wait for period;
170
171      SEL(0) <= '1'; --OPERATION: a + 1
```

```
172     SEL(2) <= '1';
173     SEL(1) <= '0'; -- RESULT = 7
174
175     wait for period;
176
177     SEL(0) <= '1'; --OPERATION: not a + 1 , 2s complement
178     SEL(2) <= '1';
179     SEL(1) <= '1'; -- RESULT = A
180
181     wait for period;
182
183
184     wait;
185 end process;
186
187 END;
188
```

Appendix E

Multiplier_VHDL.vhd

Tue Feb 02 13:58:22 2016

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    16:15:32 01/31/2016
6  -- Design Name:
7  -- Module Name:    Multiplier_VHDL - Behavioral
8  -- Project Name:
9  -- Target Devices:
10 -- Tool versions:
11 -- Description:
12 --
13 -- Dependencies:
14 --
15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.NUMERIC_STD.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx primitives in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity multiplier is
35
36 port(  a, b : in std_logic_vector(3 downto 0); --input vectors
37        c : out std_logic_vector(7 downto 0); --output
38        start: in std_logic );
39 end multiplier;
40
41 architecture Behavioral of multiplier is
42     -- state machine in order to execute the operation
43     type statetype is (state0, state1, state2);
44     signal state: statetype;
45
46 begin
47     process(a, b)
48     variable PR:std_logic_vector(7 downto 0); --PR has to be twice the size (double with
49     variable BR:std_logic_vector(4 downto 0);
50     register)
51     begin
52         case state is
53             when state0 => -- set output signals and next state
54                 if start = '1' then
55                     PR := (others => '0');
56                     state <= state1;
```

```
57         else
58             state <= state0;
59         end if;
60     when state1 =>
61         c <= "00000000";
62         state <= state2;
63     when state2 => -- same here
64         PR := "0000"&b;
65         for Z in 1 to 4 Loop
66             if PR(0) = '1' then -- if the LSB contains a 1
67                 -- add the multiplicand to the most significant half
68                 -- shift the whole register one bit to the right, throwing away the
least significant bit
69                 -- and shifting the carry bit into the MSB
70                 BR := ('0' & a) + ('0' & PR(7 downto 4));
71                 PR := BR & PR(3 downto 1);
72             else
73                 PR := '0' & PR(7 downto 1);
74             end if;
75         end Loop;
76         c <= PR; -- put PR into output, c
77         state <= state0;
78     end case;
79 end Process;
80 end Behavioral;
```

Appendix F

Multiplier_TB.vhd

Tue Feb 02 14:01:21 2016

```
1  -----
2  -- Company:
3  -- Engineer:
4  --
5  -- Create Date:    10:58:27 02/02/2016
6  -- Design Name:
7  -- Module Name:
8  -- Project Name:   Multiplier
9  -- Target Device:
10 -- Tool versions:
11 -- Description:
12 --
13 -- VHDL Test Bench Created by ISE for module: multiplier
14 --
15 -- Dependencies:
16 --
17 -- Revision:
18 -- Revision 0.01 - File Created
19 -- Additional Comments:
20 --
21 -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
23 -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
25 -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
27  -----
28  LIBRARY ieee;
29  USE ieee.std_logic_1164.ALL;
30
31  -- Uncomment the following library declaration if using
32  -- arithmetic functions with Signed or Unsigned values
33  --USE ieee.numeric_std.ALL;
34
35  ENTITY Multiplier_TB IS
36  END Multiplier_TB;
37
38  ARCHITECTURE behavior OF Multiplier_TB IS
39
40      -- Component Declaration for the Unit Under Test (UUT)
41
42      COMPONENT multiplier
43      PORT(
44          a : IN  std_logic_vector(3 downto 0);
45          b : IN  std_logic_vector(3 downto 0);
46          c : OUT std_logic_vector(7 downto 0);
47          start : IN  std_logic
48      );
49      END COMPONENT;
50
51
52  --Inputs
53  signal a : std_logic_vector(3 downto 0) := (others => '0');
54  signal b : std_logic_vector(3 downto 0) := (others => '0');
55  signal start : std_logic := '0';
56
```

```
57      --Outputs
58      signal c : std_logic_vector(7 downto 0) := (others => '0');
59      -- No clocks detected in port list. Replace <clock> below with
60      -- appropriate port name
61
62      --constant <clock>_period : time := 10 ns;
63
64  BEGIN
65
66      -- Instantiate the Unit Under Test (UUT)
67      uut: multiplier PORT MAP (
68          a => a,
69          b => b,
70          c => c,
71          start => start
72      );
73
74      -- Stimulus process
75      stim_proc: process
76      begin
77          -- hold reset state for 100 ns.
78          start <= '1';
79          wait for 10 ns;
80          start <= '0';
81          wait for 100 ns;
82          start <= '1';
83          a<= "1111";
84          b<= "1111";
85          wait for 100 ns;
86          a<= "1001";
87          b<= "1001";
88          wait for 100 ns;
89          wait;
90
91
92          wait;
93      end process;
94
95  END;
```